



IIT BOMBAY

CS 254

DIGITAL LOGIC DESIGN

---

# Streaming Colour Interpolater

---

Mar '16

Team : kuchbhi

Name	Roll No.
Srajan	140050017
Shrey	140050018
Rishabh	140050019
Anuj	140050024

# 1 Introduction

Our project deals with implementing a streaming colour interpolator. Interpolation can be thought of as a smooth transition between two colors, which can be created using a linear mixture of the respective colour coordinates. In layman's terms the interpolation will basically smooth out the image.

## 2 Specifics

For this project we are dealing with 16 bit colours. Each pixel of the image is defined by three 16 bit colours. (Red, Green & Blue) The interpolation algorithm states:

$$r_{x,y} = R.r_{x,y} + \frac{1-R}{4} \cdot (r_{x+1,y} + r_{x-1,y} + r_{x,y+1} + r_{x,y-1}) \quad (1)$$

$$g_{x,y} = G.g_{x,y} + \frac{1-B}{4} \cdot (g_{x+1,y} + g_{x-1,y} + g_{x,y+1} + g_{x,y-1}) \quad (2)$$

$$b_{x,y} = B.b_{x,y} + \frac{1-G}{4} \cdot (b_{x+1,y} + b_{x-1,y} + b_{x,y+1} + b_{x,y-1}) \quad (3)$$

where,

$r_{x,y}$  is the 16-bit value of the red colour at position (x,y)

$R, G, B$  are the 16-bit constants of interpolation

## 3 Input & Output

### Input Signals :

- Three 16-bit inputs representing the Red, Blue and Green values
- One 1-bit input for the Reset signal
- One 1-bit input for the Start signal

### Input description :

Reset input is held high for two clock cycles to reset the system. Start is held high for two clock cycles to indicate the start of system. Also, at this time system will be provided with three constants R, B and G via the three 16-bit inputs. The actual values for the interpolation constants are the R, G, B values divided by  $2^{16}$ .

After this, system will be provided with three 16 bit integers representing RGB values of the pixel at x,y at each clock. The input values of pixel follow a to and fro oscillatory pattern, while moving from top to bottom.

For all the pixels which do not have neighbours, take adjacent values to be zeros. Also, for our project the image size is 100 x 100 pixels.

### Output Signals :

- Three 16-bit outputs representing the Red, Blue and Green values
- One 1-bit output for the validity signal

### Output description :

Only when the validity bit is high, the 48-bit output should be considered. The system will start outputting the pixel values in the same order as the input in 200 clock cycles from the start.

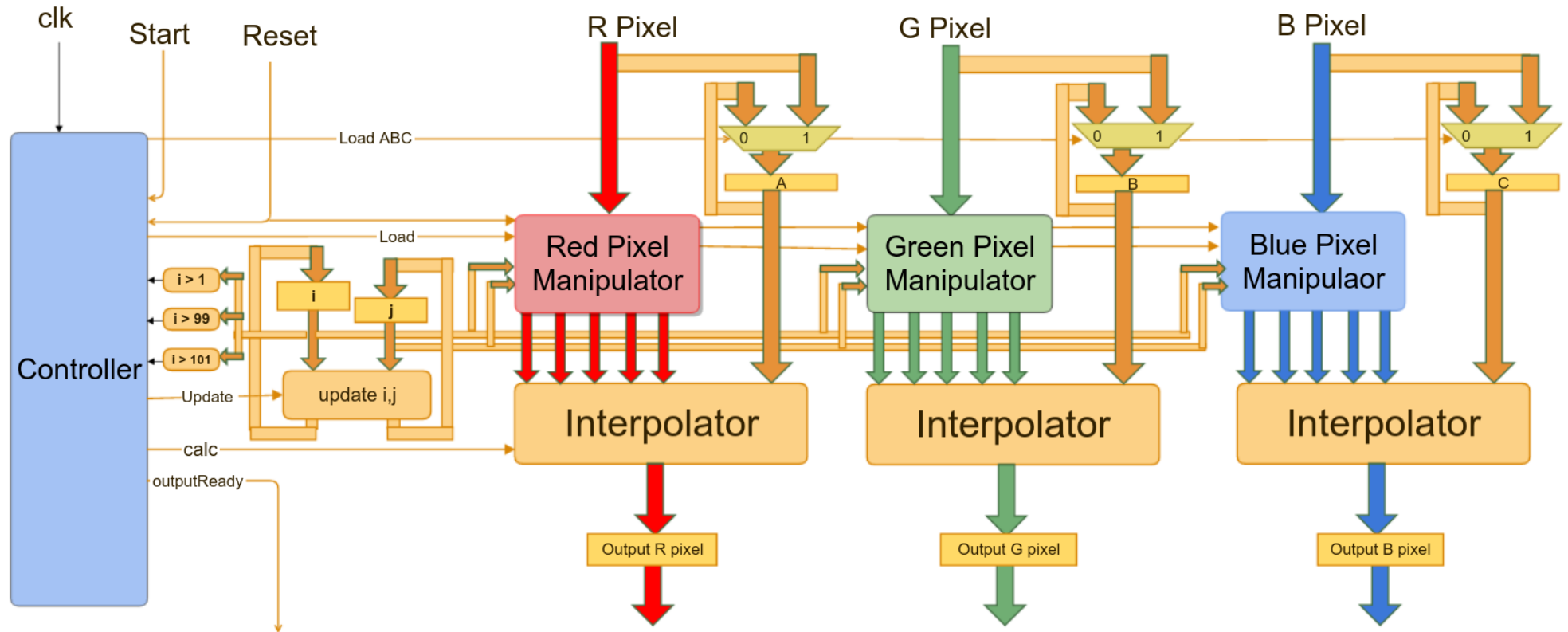


Figure 1: Stipulated datapath diagram

## 4 Pixel Manipulator

It consists of 4 vectors (numbered 0 through 3) consisting of 100 elements each where each element is a 16-bit number storing the pixel value. Everywhere,  $i$  refers to the vector/row number, and  $j$  refers to the element number in that vector.

### 4.1 Inputs

When load is high, it reads 16-bits of Red/Green/Blue pixel from the input and also takes in the value of  $i$  and  $j$  from registers and reset and load from the controller.

### 4.2 Functioning

- When reset is high, it sets all the entries in the vectors to 0
- When load is high, it updates the  $j^{\text{th}}$  entry of the  $i^{\text{th}}$  vector to the 16-bit pixel value it takes as input
- When load is low, it updates the  $j^{\text{th}}$  entry of  $i^{\text{th}}$  vector to 0

Note : Everywhere, the arithmetic in ' $i$ ' occurs in modulo 4.

### 4.3 Outputs

- It outputs 5 16-bit values used by the calculator
- One of these 16-bit values is the current pixel value being processed ( $j^{\text{th}}$  pixel in  $i\text{-}2^{\text{th}}$  vector)
- Rest of the 4 values are of the adjacent pixels (which will be taken to be 0 in case they don't exist)

## 5 Interpolator

### 5.1 Inputs

It takes in five 16-bit numbers ( $C, u, d, l, r$ ) from the pixel storer and another 16-bit number ( $K$ ) as input.

where,

$C$  is the pixel value for which interpolated value is to be calculated

$K$  is the constant for interpolation and is equal to R, B or G respectively

$u, d, l, r$  are the pixel value of the adjacent cells (0 if they don't exist)

### 5.2 Outputs

- When 'calc' signal from controller is low, its output is 0
- Otherwise, it outputs the interpolated pixel value which is calculated as below

$$\text{output} = \text{round}\left(K \cdot C + \frac{(2^{16} - K) \cdot \frac{u+l+d+r}{4}}{2^{16}}\right) \quad (4)$$

- This will use Full adders, Multipliers and Right Shifters.

## 6 Updater (i, j)

### 6.1 Inputs

It takes i & j input from the registers and the ‘update’ input from the controller.

### 6.2 Outputs

It outputs two integers corresponding to updated value of i & j. Basically it calculates them on the basis of traversal in the vectors inside the Pixel Manipulators.

```
if update = 0:
    updated_i = 0
    updated_j = 0
else:
    if j = 99:
        updated_i = i + 1
        updated_j = j + 1
    else :
        updated_i = i
        updated_j = j + 1
```

## 7 Pseudo Code

This is the software implementation of our interpolation algorithm. The actual hardware implementation may vary. This is only for the red colour, it can be easily extended to the whole pixel.

```
if reset = 1:
    set all of i, j, calc to 0
    set all values stored in pixel manipulator to 0

if start = 1:
    read value of A,B and C

while (i < 102):
    if (NOT i > 99):
        # read pixel values of RGB pixel and update jth entry of
        # ith vector in all the three manipulators
    else:
        set jth entry of ith vector in all the three manipulators to 0

    RC = jth entry in (i-2)th vector in red pixel manipulator
    Ru = (99 - j)th entry in (i-3)th vector in red pixel manipulator
    Rd = (99 - j)th entry in (i-1)th vector in red pixel manipulator
    Rl = (j == 0) ? 0 : (j-1)th entry in (i-2)th vector in red pixel manipulator
    Rr = (j == 99) ? 0 : (j+1)th entry in (i-2)th vector in red pixel manipulator

    if (i > 2 AND NOT i > 101):
        outputReady = 1
        interpolated_R_pixel = round((R*RC + (2^16 - R)*((Ru + Rd + Rl + Rr)/4))/2^16)

    if (i > 101):
        outputReady = 0
```

Note : Everywhere, the arithmetic in ‘i’ occurs in modulo 4.

## 8 State Diagram

In the initial state (given by state variable 0000), the reset is assumed to be high and start is assumed to be low. This resets all the registers to zero and the controller variables 'update', 'LoadABC' and 'Low' are also low and the circuit is ready to start processing a stream of pixels. After one clock cycle, the reset still remains high and start remains zero indicating state 0001.

In the next clock cycle, the start input becomes high and reset becomes low which corresponds to state 0010. The reset variable is assumed to remain low throughout afterwards. The start input remains high even after one clock cycle and the controller makes LoadABC signal high in the state 0011. When LoadABC signal becomes high, the coefficients iA, iB and iC are taken as input from the stream.

In the next clock cycle, the start and reset are both assumed to be low and the controller variable update becomes high. The update variable is an input to the block 'Update i,j' which appropriately updates i and j. This variable is a function of load and the controller inputs i  $\leq$  101. Also, the variable 'Load' becomes high representing the fact that the first pixel values are fed into the inputs. These changes lead to a transition to state 0100.

Now, the variable 'Update' remains high throughout until i exceeds 101. If the value of i does not exceed 1, the state remains same and this means that the circuit is taking input only. Therefore, the controller remains in this state for the 200 clock cycles (until the first 200 pixels are read). As soon as i exceeds 1, i.e. i becomes equal to 2, the state changes to 0101. Also, the controller output calc is set high in this state representing that the interpolater block start processing the pixels. At this state, there are two processes happening, some pixel value is read and the required value for the pixel which was read 200 clock cycles before this pixel is computed.

In the next clock cycle, there is a transition to state 0110 where OutputReady variable becomes high denoting that the value at the output is valid. Thus, there is a delay of 201 clock cycles between the time of reading the first pixel and the time at which the first interpolated RGB value is ready to be output. The controller's state doesn't change until 'i' exceeds 99. When i exceeds 99, i.e. after 10000 clock cycles when we started reading the input pixels, the state changes and in this state, the variable 'Load' is zero as there are no more input pixels to feed to the circuit. For the next 200 clock cycles, when i does not exceed 101, the controller's state remains the same.

As soon as i exceeds 101, all but last interpolated values are computed and thus the variable 'calc' is set to 0 which will get updated in the next state. The last interpolated value gets computed in this cycle and therefore OutputReady remains high in this state. In the next clock cycle, the outputReady is set to 0 which will get Updated in the next clock cycle. Also, during this cycle, the output of last interpolated value is done. In the final state, OutputReady is set to 0 as the output of all the interpolated values is done.

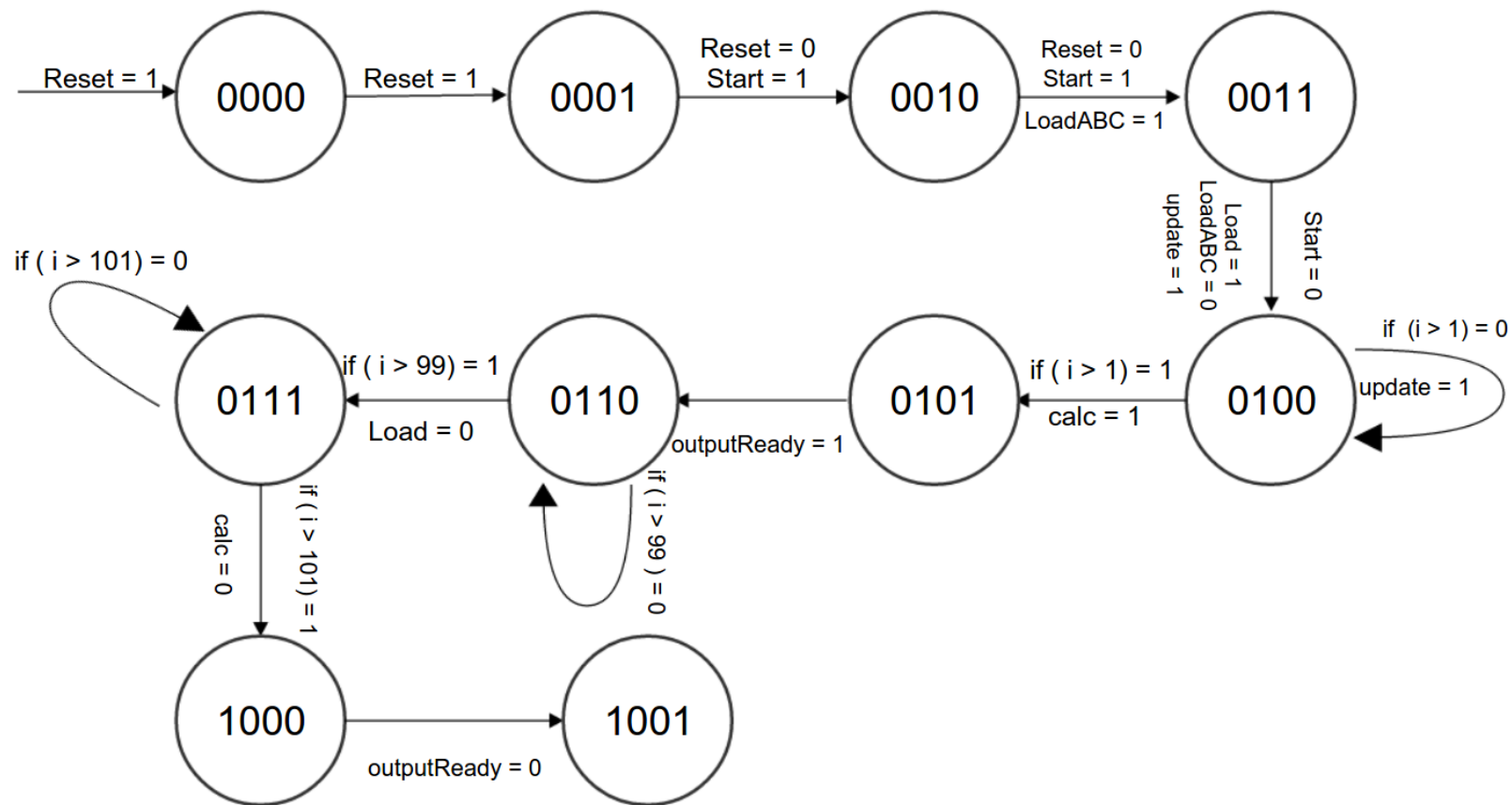


Figure 2: Stipulated state diagram

## **9 Testing & Verification**

We plan to test this program against real 100x100 images. We will convert them into RGB pixels and input them into our program, and do the reverse on the output of our program. Thus we can compare the the output image to see if it was correctly interpolated. This is an additional goal, and not part of our core project.

## **10 Distribution of work**

Datapath will be implemented by Anuj Mittal and Shrey Rajesh. This includes implementing and testing all the black boxes i.e Pixel Manipulator, Interpolator and Updater block.

Controller circuit will be handled by Srajan Garg and Rishabh Agarwal. They will also do the verification and testing for the program by generating testbench from actual image data (hex dump) and qualitative analysis of program (blurring effect).

Preparation of test cases will be done by all the team members and the above tasks are also done in collaboration with other team members but the mentioned team members will mainly be responsible for above tasks.